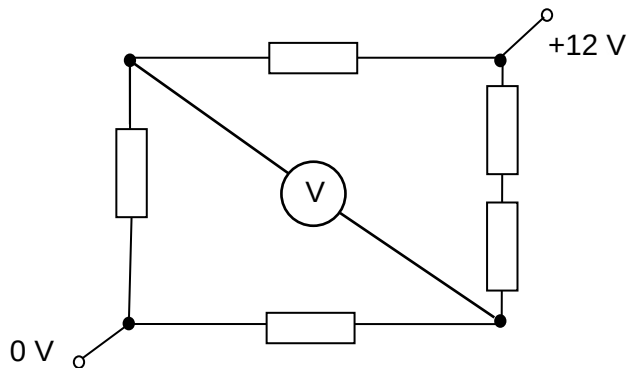


- 20** In the circuit shown, all the resistors have the same resistance. The voltmeter can be assumed to be ideal.



The potential difference between the terminals is 12 V.

What is the reading on the voltmeter?

A 0 V

B 2 V

C 4 V

D 6 V