

		from the electric field line, the lesser is the electric potential due to the positive charge.
22	B	The circuit is equivalent to 2 sets of parallel resistors in series with each other. $\text{Effective resistance} = \left(\frac{1}{R} + \frac{1}{R} \right)^{-1} \times 2$ $= R$
23	D	Total potential drop from 1 to 4 = $2 IR$ where I is the current through series resistors