

18	A Resistance, $R = \frac{\rho l}{A}$ and potential drop across each wire $V = IR = I \left(\frac{\rho l}{A} \right) = I \rho \left(\frac{l}{A} \right)$ Since current and resistivity are constants, the potential drop increases with distance from X (i.e. length of wire in this case), and the smaller the cross-sectional area A, the larger is the drop per unit length of wire. So the last segment has the largest potential drop per unit length.
19	C