
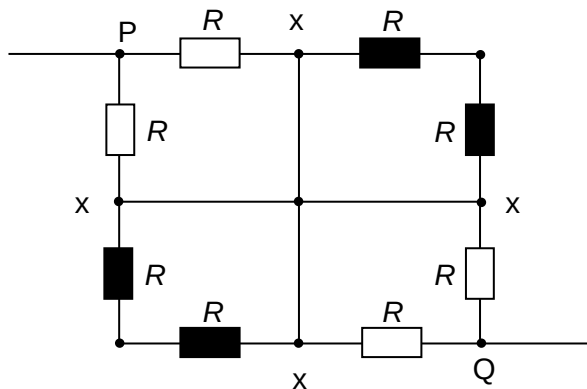


19


C

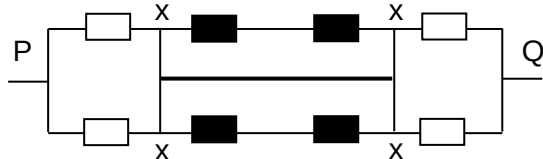

The above circuit can be redrawn as:



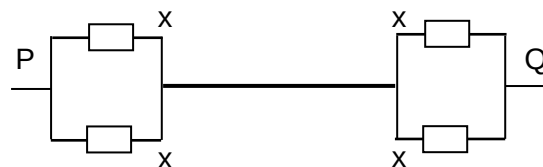No current passes through the resistors in black as all current will pass through the bold wire (zero resistance).



This simplifies the circuit to a series connection of two sets of parallel resistors. So resistance across PQ = $R/2 + R/2 = R$