

17	Answer: B
	Applying potential divider principle, the potential difference <u>across</u> the variable resistor, V_R varies between: $V_R = \left(\frac{100}{100 + 500} \right) 30 = 5V \quad \text{to} \quad V_R = \left(\frac{500}{500 + 500} \right) 30 = 15V$

