

18	Answer: D
	A and B are wrong because the diode is connected in reverse-bias. When temperature of the thermistor is low, resistance is high and hence p.d. across the thermistor is high. The heater should be connected across the thermistor.

19	Answer: A
-----------	------------------