

22

B

Resistance of each of the lamp : $R = \frac{V_{rating}^2}{P_{rating}}$

since, both of them have the same voltage rating: $\frac{R_A}{R_B} = \frac{P_{rating,B}}{P_{rating,A}} = \frac{40}{10} = \frac{4}{1}$

Since, both lamps are connected in series, the same current passes both lamps and power emitted by each lamp : $P_{emitted} = I^2 R$.

$$\frac{P_{emitted,A}}{P_{emitted,B}} = \frac{R_A}{R_B} = \frac{4}{1} \Rightarrow P_A = 4P_B$$

23	A	Consider the secondary circuit: when temperature is low the resistance of the thermistor is high. This means
----	---	--