

		from the disc's perspective.
26	B	Using the potential divider principle, potential difference across the secondary coil = $80 \times \left(\frac{1500}{1000}\right) = 120V$ Current passing through the secondary coil = $I = \frac{V}{R} = \frac{80}{1000} = 0.080A$ Power dissipated by secondary coil = $IV = 0.080 \times 120 = 9.60W$ Potential difference across the primary coil = $120 \times \frac{200}{500} = 48.0V$ Power dissipated by primary coil = $V_p I_p = 9.60 \rightarrow I_p = \frac{9.60}{48.0} = 0.20A$
27	C	