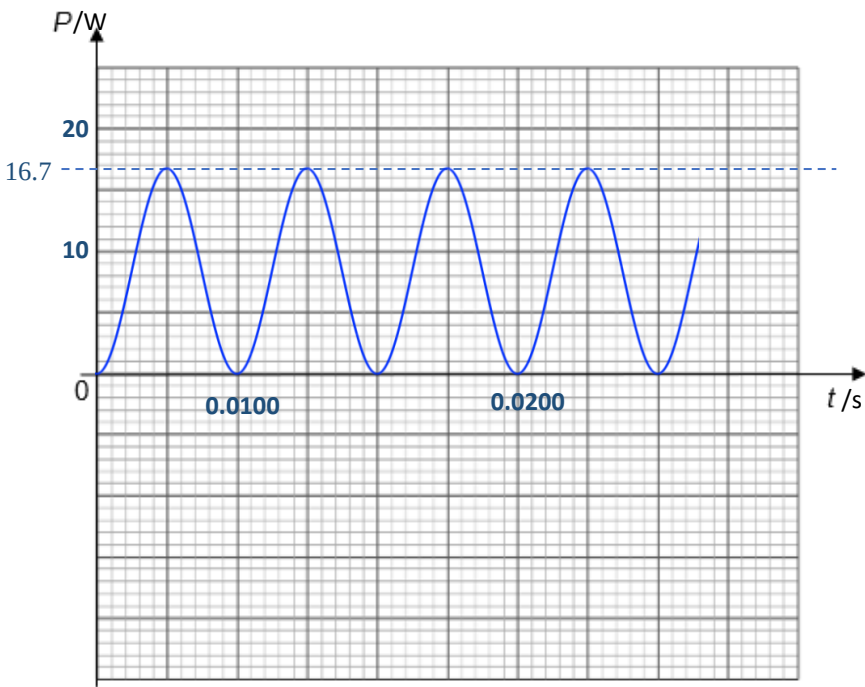


Q5		
(a)(i)	$\omega = \frac{2\pi}{T} = 628 \Rightarrow T = 1.00 \times 10^{-2} \text{ s}$	A1
(a)(ii)	$V_{rms} = \frac{V_0}{\sqrt{2}} = \frac{15}{\sqrt{2}} = 10.6 \text{ V} = 11 \text{ V}$	A1
(a)(iii)	$\frac{1}{R_{eff}} = \frac{1}{12.0} + \frac{1}{3.0 + 6.0} = \frac{7}{36} \Rightarrow R_{eff} = 5.1429 \Omega$	M1
	$I_0 = \frac{V_0}{R} = \frac{15}{5.1429} = 2.92 \text{ A} = 2.9 \text{ A}$	A1
(a)(iv)	$V_{rms} \text{ across } 6.0 \Omega \text{ resistor} = \frac{V_0}{\sqrt{2}} = \frac{(15 \times \frac{6.0}{9.0})}{\sqrt{2}} = \frac{10.0 \text{ V}}{\sqrt{2}} = 7.071 \text{ V}$	M1
	$\text{Mean power} = \frac{V^2}{R} = \frac{7.071^2}{6.0} = 8.33 \text{ W} = 8.3 \text{ W}$	A1
(b)	 $P_0 = 8.33 \times 2 = 16.7 \text{ W}$	
	<i>B1 : Correct shape ($\sin^2$ graph)</i> <i>B1: at least 2 cycles shown with period labelled correctly ($t \geq 2T$ i.e. 4 maximum power in graph)</i> <i>B1: correct peak value labelled on graph.</i>	B3

06		
----	--	--