

Q24 When the current is flowing from X to Y, the effective resistance of the circuit is $2.0\ \Omega$, and when the current is flowing from Y to X, the effective resistance of the circuit is $3.0\ \Omega$.

Hence, the peak currents will be different when the current is flowing from X to Y and from Y to X.

Answer: D

Q25 Peak voltage in secondary coil is 90 V