

		zero at that point. But the value of the potential at that point need not be zero.
22	B	From graph, when current is 40 mA, p.d. is approximately 1.2 V. Therefore, p.d. across resistor = $6.0 - 1.2 = 4.8 \text{ V}$ $R = V/I = (4.8)/(0.040) = 120 \text{ } \Omega$

23	D	
----	---	--