

|    |   |                                                                                                                                                                                                                                                                           |
|----|---|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| 26 | A | $\frac{V_s}{V_p} = \frac{N_s}{N_p}$ $\frac{V_s}{120} = \frac{1}{60}$ $V_s = 2.0 \text{ V}$ <p>Then <math>I_s = V_s/R = 2.0/3.0 = 0.667 \text{ A}</math></p> <p>For ideal transformer,</p> $V_p I_p = V_s I_s$ $120 \times I_p = 2.0 \times 0.667$ $I_p = 0.011 \text{ A}$ |
| 27 | C | The range of wavelengths for visible light is 400 nm to 700 nm                                                                                                                                                                                                            |