

		$\frac{P}{Q} = \frac{V^2/R}{V^2/R} = 1$
	21	C There is no difference between the connections in diagram 1 and diagram 2. Since the lamps are of the same resistance, putting a wire across the points parallel to the lamps P and Q does nothing to change the circuit itself
	22	D Total energy provided by battery is 60 J