

		inner loop is constant and the current in the inner loop is constant.
27	B	Clockwise: current pass through $200 \text{ } \Omega$ only. anticlockwise: current pass through both resistors.
28	C	Photocurrent is proportional to intensity