
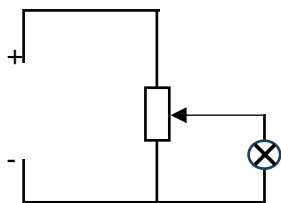


- 21 A lamp is connected to a power supply of negligible internal resistance. Which circuit could not be used as a practical means to vary the voltage across the lamp?


A

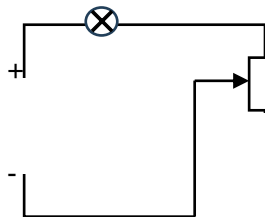


B



C

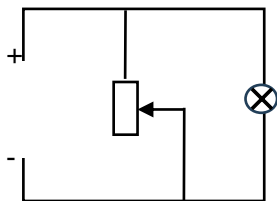

D

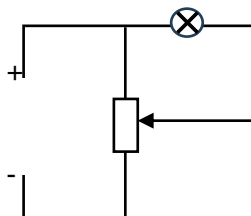

Ans: C

Options A, B & D allow adjusting the slider to vary the voltage across.

Option C connect directly between the terminals of the cell.

22 Five resistors, each of $50\ \Omega$, are connected in a loop as shown below. A 10.0 V battery of zero