

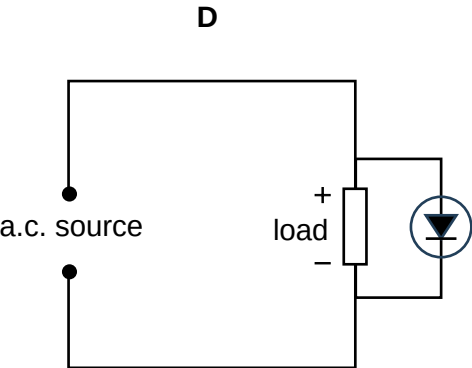
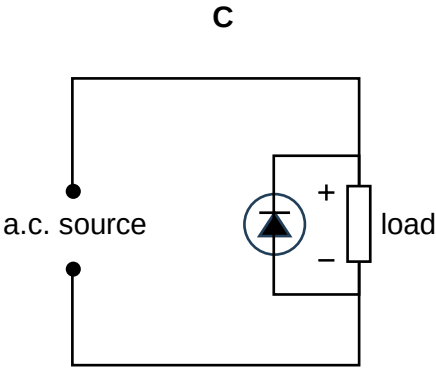
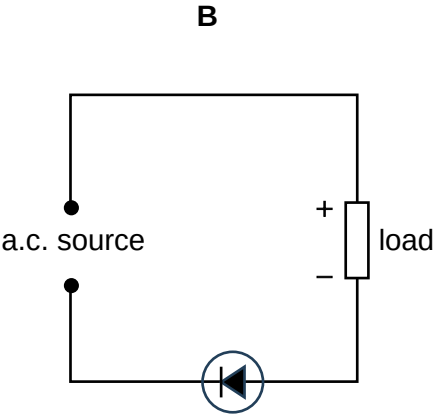
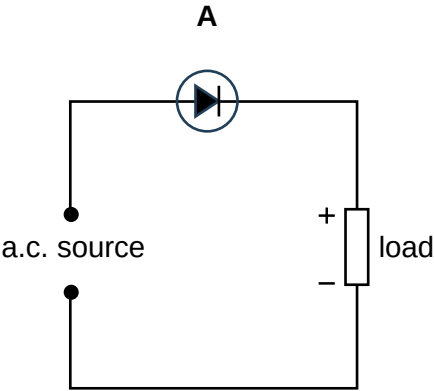


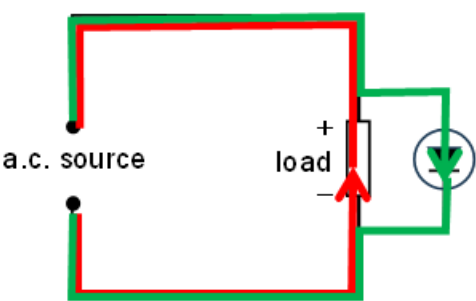26 An a.c. source can be rectified to supply a d.c. to a load using a semiconductor diode, which is assumed to ideal. Which of the following circuits will not correctly supply the required d.c. to the load?



Ans: D

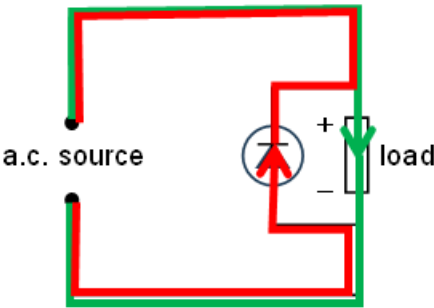

27 In a photoelectric cell experiment sodium (Na) metal is exposed to electromagnetic radiation of