

- 4 (a) A circuit is set up as shown in Fig. 4.1. Cell A has an electromotive force (e.m.f.) of 2.0 V and negligible internal resistance. XY is a uniform wire of length 100.0 cm and resistance

5.0 Ω