

|    |   |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                 |
|----|---|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
|    |   |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                 |
| 23 | A | $I = \frac{E}{R} = \frac{E}{\frac{\rho L}{A}} = \frac{EA}{\rho L} = \frac{E\pi(d/2)^2}{\rho L} \frac{\pi d^2 E}{4\rho L}$ <p>Hence <math>I \propto \frac{d^2}{\rho}</math> since <math>L</math> and <math>E</math> across the wires in parallel are constants.</p> $\frac{I_X}{I_Y} = \frac{d_X^2}{\rho_X} \times \frac{\rho_Y}{d_Y^2} = \frac{\left(\frac{1}{4}d_Y\right)^2 \times \rho_Y}{d_Y^2 \times \frac{1}{2}\rho_Y} = \frac{2}{16} = \frac{1}{8}$ $\frac{I_X}{I_{total}} = \frac{1}{9}$ |

**Raffles Institution**  
**Year 5-6 Physics Department**

**24**

**D**

Since ammeter reading is zero, there is also no current in the middle wire joining the