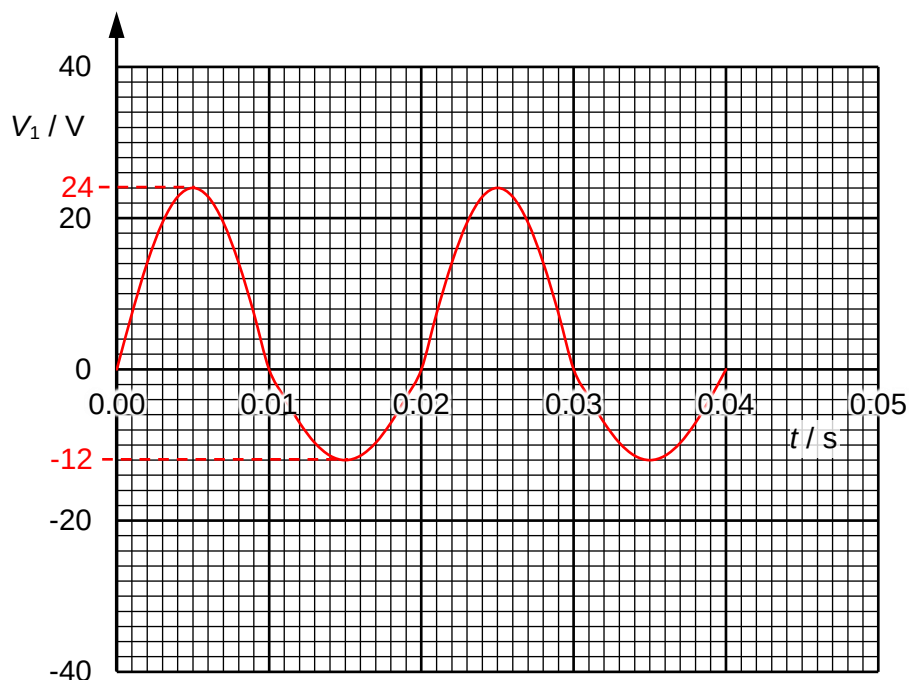


- 6 (a) The root-mean-square value of an alternating current is that value of the direct current that would produce thermal energy at the same rate in the same resistor.

(b) (i)



With S closed, current passes through the diode and  $R_1$  in the forward bias direction. In the reverse bias direction, current passes through  $R_1$  and  $R_2$ .


Forward bias: peak  $V_1 = \text{peak } V = 24 \text{ V}$

Reverse bias: peak  $V_1 = 12 \text{ V}$

$$\text{period } T = \frac{2\pi}{\omega} = \frac{2\pi}{314} = 0.02 \text{ s}$$

\*Sine graph with correct period.

(ii)

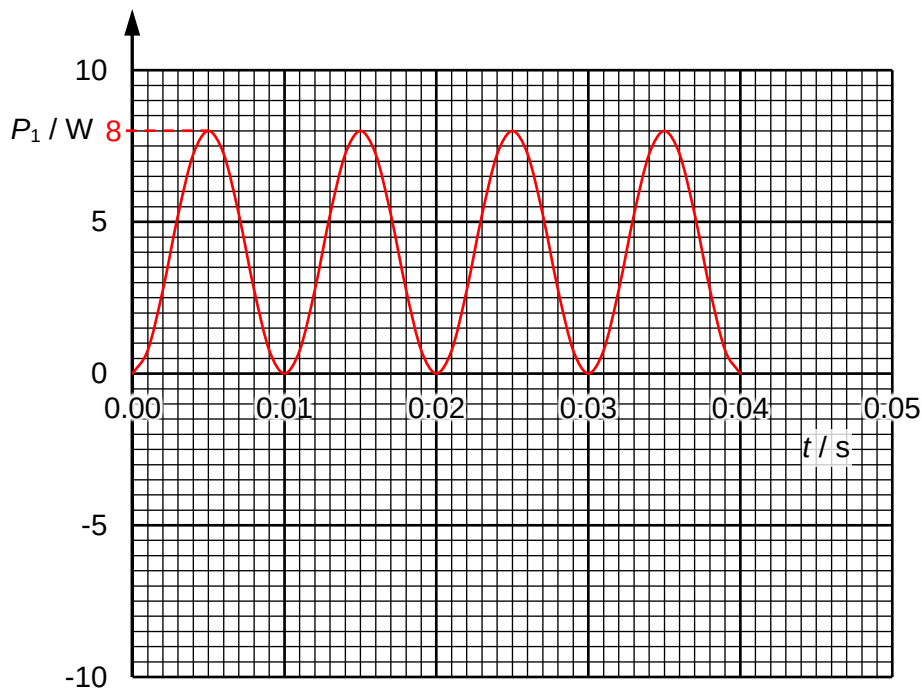

**Raffles Institution**  
**Year 5-6 Physics Department**

With S opened, current passes through  $R_1$  and  $R_2$  all the time and does not pass through the diode.

Since  $V$  and  $I$  of the alternating supply is sinusoidal, power graph will be a  $\sin^2$  graph.

$$\text{peak } P_1 = \frac{(\text{peak } V_1)^2}{R_1} = \frac{(24/2)^2}{18} = 8 \text{ W}$$

\*Correct shape (smooth curve, sine squared) with correct period.

**Raffles Institution**  
**Year 5-6 Physics Department**

3 (a) The emission line spectrum consists of a series of distinct lines of specific colours/