

	(a)	(b)
24.	Ans: C $current = \frac{P}{V} = \frac{120000}{6000} = 20 A$ $power\ dissipated\ in\ wire = (20)^2(3.0) = 1200 W$	
25.	Ans: A	