

21 Ans: B

SAJC Prelims 2024

9749/01

[Turn Over

If current in Y is I , then current in F is $2I$, so current in C is $3I$

Let the resistance of one resistor be R ,

$R_{AB} = (1/1 + 1/2)^{-1} R = 2/3 R$, so $R_{C+AB+D} = 1 + 2/3 + 1 = 8/3 R$

Since current in R_{C+AB+D} is $3I$, then current in E is $8I$

so current in X = $3I + 8I = 11I$

