

6(a)(i)	From the graph, $R = 80 \, \Omega$, $T = 40 \, \Omega$ at 120°C $E = I R_T$ $3.0 = I (80 + 40)$ $I = 25 \times 10^{-3} \text{ A} = 0.025 \text{ A}$	[1] [1]																							
(ii)	(When the temperature increases from 0°C to 75°C , magnitude of RATE of Increase of resistance of R is smaller than the magnitude of RATE of Decrease of resistance of T .} {Compare their gradients} Thus, effective resistance decreases at a decreasing rate with respect to temperature.	[1]																							
(iii)	From graph at 30°C , resistance of $R = 55 \, \Omega$ and resistance of $T = 110 \, \Omega$ By potential divider rule, p.d. across $T = (R_T / R_{\text{total}}) \times 3.0 \text{ V} = (110/110+55) \times 3.0 = 2$	[1] [1]																							
(b) (i)	faulty lamp: lamp E nature of fault: lamp fused/ fuse melt/broken filament	[1] [1]																							
(ii)	Resistance of one non-faulty lamp = $30.0 / 2 = 15.0$	[1]																							
(iii)	<table border="1"><thead><tr><th colspan="3">switch</th><th rowspan="2">ohm-meter reading / Ω</th></tr><tr><th>S_1</th><th>S_2</th><th>S_3</th></tr></thead><tbody><tr><td>open</td><td>open</td><td>open</td><td>∞</td></tr><tr><td>closed</td><td>open</td><td>open</td><td>30.0</td></tr><tr><td>closed</td><td>closed</td><td>open</td><td>25.0</td></tr><tr><td>closed</td><td>closed</td><td>closed</td><td>15.0</td></tr></tbody></table>	switch			ohm-meter reading / Ω	S_1	S_2	S_3	open	open	open	∞	closed	open	open	30.0	closed	closed	open	25.0	closed	closed	closed	15.0	- 1 mark for each mistake
switch			ohm-meter reading / Ω																						
S_1	S_2	S_3																							
open	open	open	∞																						
closed	open	open	30.0																						
closed	closed	open	25.0																						
closed	closed	closed	15.0																						

