

Q18 Ans: B

Note that the middle resistor is redundant as the pd across it is the same, hence no current flow.

$$\text{Hence } R_E = \left(\frac{1}{R+R} + \frac{1}{R+R} \right)^{-1} = R$$

Q19 Ans: C