

**Q19 Ans: C**

$$R_{\text{eff across PQ}} = \left( \frac{1}{20} + \frac{1}{8+3} \right)^{-1} = 7.10 \, \Omega$$

$$V_{PQ} = \frac{R_{PQ}}{R_{PQ} + R_{10\Omega}} \times 6.0 = \frac{7.10}{7.10 + 10} \times 6.0 = 2.5 \, \text{V}$$

**Q20 Ans: A**