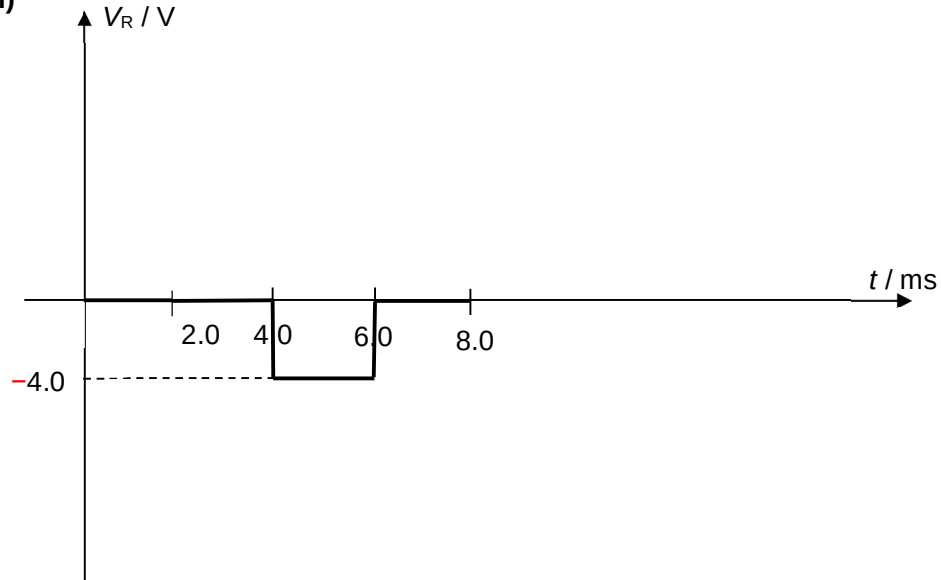


6	(a)	(i)	$V_{\text{rms}} = \sqrt{\frac{2(5.0)^2(2.0) + 2(10.0)^2(2.0)}{8.0}}$ $= 7.9 \text{ V}$	[M1] [A1]
		(ii) 1.	0 V	[A1]
		(ii) 2.	p.d. across resistor $R = -10.0 + 6.0$ $= -4.0 \text{ V}$ OR $+4.0 \text{ V}$	[M1] [A1]

(iii)



1 mark for shape of graph.

1 mark for labelled axes (values of V_R if graph is correct)Allow $+4.0 \text{ V}$

(b)	Transmission voltage can be stepped up [B1], thereby minimising power loss [B1].
-----	--

7	(a)	$^{226}\text{Po} \rightarrow ^{222}\text{Pn} + ^4\text{He}$	
---	-----	---	--