

		$u_Q = 1.00$
21	D	$E = 3r + 3(1)$ $E = 2r + 2(2)$ solving, $E = 6.0 \text{ V}$
22	B	Since the galvanometer reads zero when $PS = 40.0 \text{ cm}$