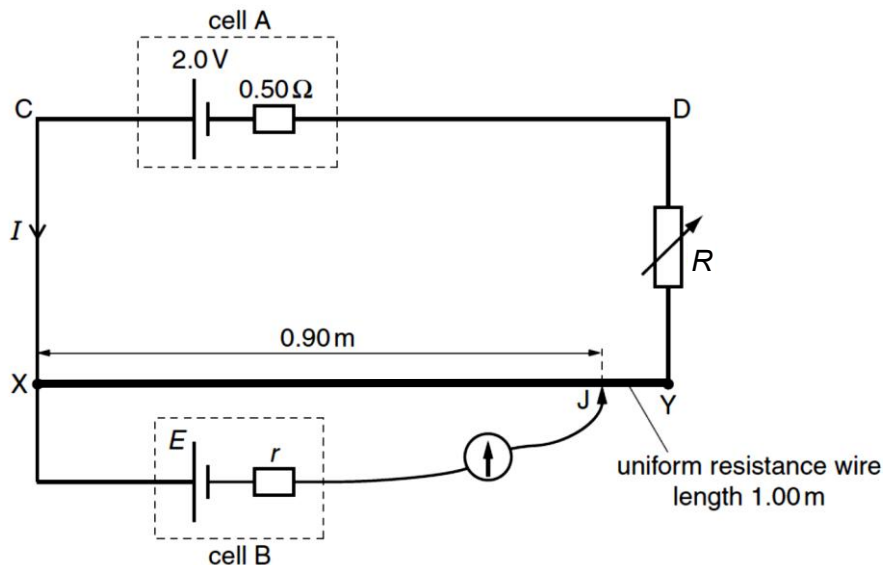


- 22 The circuit shown below is used to compare potential differences.



Which of the following statements is **false** ?

- A The value of the internal resistance of cell B is required for the determination of e.m.f. of cell B.
- B Increasing the internal resistance of cell A increases the balance length XJ.
- C Potential difference across XJ is always equal to e.m.f. of cell B at balance point.
- D Potential difference across XJ is $\frac{9}{10}$ of the potential difference across XY.