

- 26** In an ideal transformer, the ratio of the secondary turns to the primary turns is 1:60. A 120 V a.c. source is connected to the primary coil and a $3.0\ \Omega$ resistor is connected to the secondary coil.

What is the current in the secondary coil?

- A** 0.011 A **B** 0.67 A **C** 2.0 A **D** 40 A