

20 A lamp of resistance R is powered by an electrical source with internal resistance r .

Which expression gives the fraction of the total power dissipated in the electrical source?

A $\frac{r}{R+r}$

B $\frac{r}{R}$

C $\frac{R}{R+r}$

D 1

21 The diagram shows four identical lamps connected in a circuit with a power supply