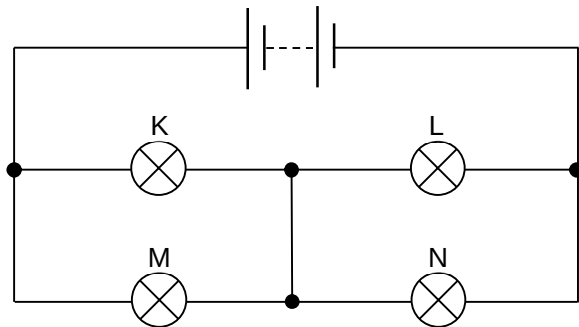


21 The diagram shows four identical lamps connected in a circuit with a power supply.



What happens when the filament of lamp K breaks?

- A** Lamp M will not light up.
- B** Lamp L will be brighter than before.
- C** Lamp M will be brighter than before.
- D** Lamp L and N will remain as bright as before.

22 In the circuit shown, all the resistors have the same resistance, and all the ammeters have