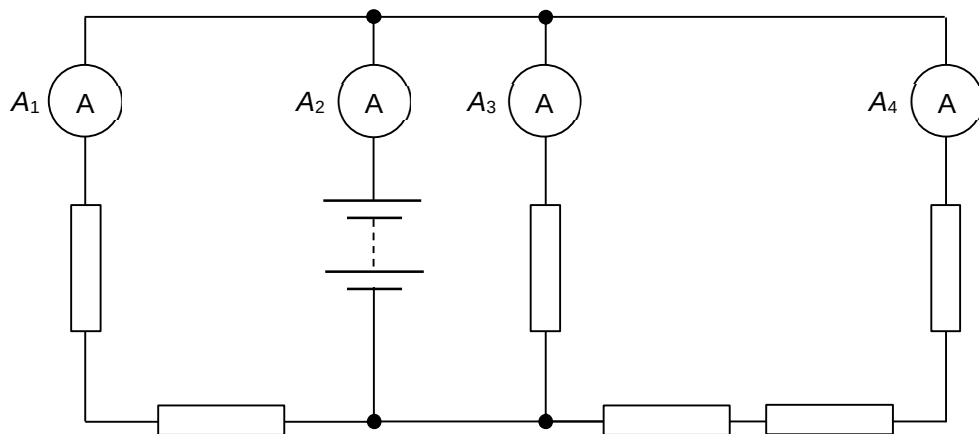


- 22 In the circuit shown, all the resistors have the same resistance, and all the ammeters have negligible resistance.



The reading A_1 is 0.6 A.

What are the readings on the other ammeters?

	A_2 / A	A_3 / A	A_4 / A
A	1.0	0.3	0.1
B	1.4	0.6	0.2
C	1.8	0.9	0.3
D	2.2	1.2	0.4

23 A narrow parallel beam of charged particles, each with speed v , passes through a slit S_1 .