

22 Compare left branch and centre branch: Reading $A_3 = 2(0.6) = 1.2 \text{ A}$

Compare centre branch and right branch: Reading $A_4 = \frac{1.2}{3} = 0.4 \text{ A}$

Current from battery: $A_2 = 0.6 + 1.2 + 0.4 = 2.2 \text{ A}$

Answer: D