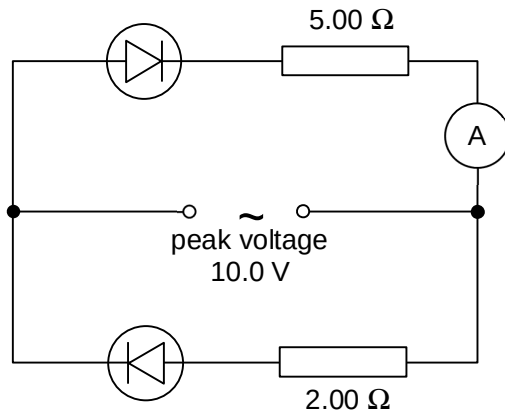


- 27** A sinusoidal alternating supply of peak voltage 10.0 V is connected to two diodes, two fixed resistors and an ammeter as shown.



What is the root-mean-square value of the current detected by the ammeter?

- A** 1.00 A
- B** 1.41 A
- C** 2.24 A
- D** 2.50 A

- 28** A sinusoidal alternating supply is connected to a $10\ \Omega$ resistor in series. The graph shows