

- 7 Fig. 7.1 shows an ideal transformer, where the primary coil is connected to an alternating voltage supply of 20 V. The secondary coil is connected to an ideal ammeter and a fixed resistor R of resistance $50\ \Omega$. The number of turns in the primary coil N_P is 25.

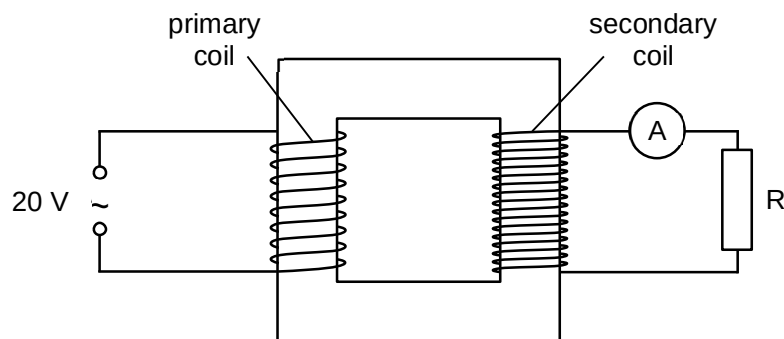


Fig. 7.1

Fig. 7.2 shows the variation of the current I with time t recorded from the ammeter.

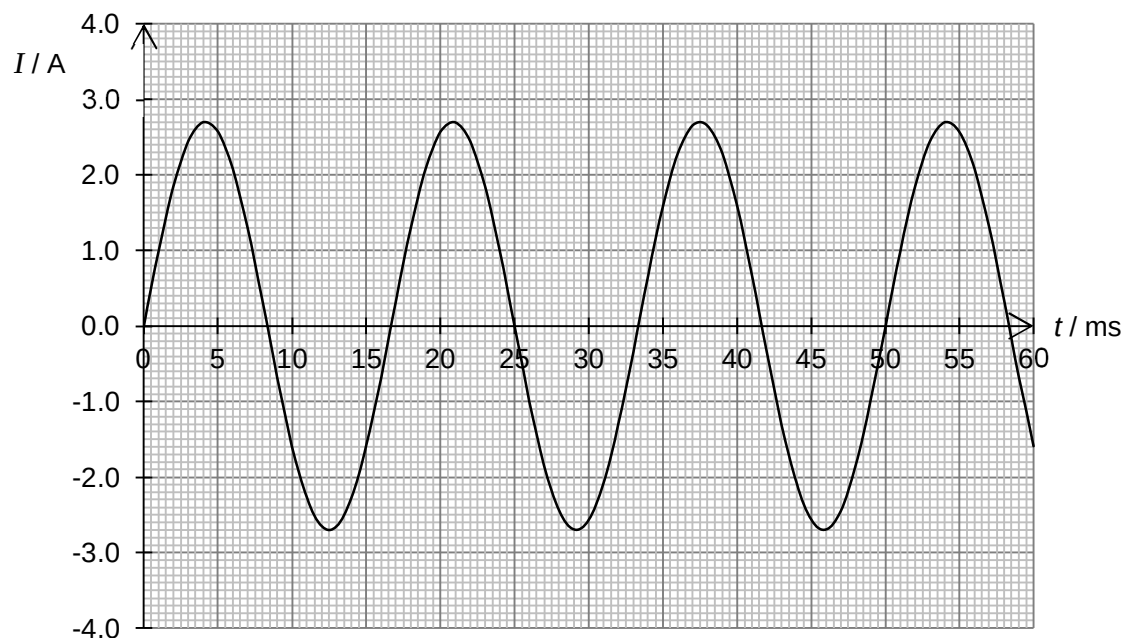


Fig. 7.2

- (a) Determine the mean power dissipated across the resistor R.

mean power = W [2]

(b) Determine the number of turns in the secondary coil N_s .

$N_s = \dots\dots\dots$ [3]

(c) Determine the frequency of the alternating voltage supply.

frequency = $\dots\dots\dots$ Hz [2]

(d) Explain how your answer in **(a)** will be affected if the frequency of the alternating voltage supply is doubled.

$\dots\dots\dots$
 $\dots\dots\dots$
 $\dots\dots\dots$ [2]

18

Section B

Answer **one** question from this section.

8 (a) Fig. 8.1 shows part of the orbit of a space capsule around the Earth.