

26	A A: By using the relationship above, when the number of turns in the primary coil N_p is increased, the p.d. across the secondary coil V_s will decrease. $V_s/V_p = N_s/N_p$ B: Increasing the cross sectional area does not affect the p.d. across the secondary coil. C: Increasing the resistance across the variable resistor only reduces the current in secondary coil (not the p.d. across it). D: Decreasing the resistance across variable resistor only increases the current in secondary coil (not the p.d. across it). $V_s/V_p = I_p/I_s$
27	D