

$$(9.6 \rightarrow 3.2)$$

22 Resistance of thermistor increases when temperature of thermistor is reduced.

Hence, in circuit D, the ratio of resistances of thermistor and fixed resistor increases.

Hence, the ratio of potential differences of thermistor and fixed resistor increases (potential divider principle) (i.e. potential difference across thermistor is now a higher fraction of the emf).

Hence potential difference across thermistor (voltmeter reading) increases.

23 Voltage is constant $\rightarrow V = IR$