

- 23 B** Option A: Student thought that no current flows through hence potential drop must be zero across all the bulbs in the circuit.
Option B: Correct.
Option C: Student did not consider the potential difference across A and thought that the potentials across bulb D is the same.
Option D: Student did not consider the potential difference across A.

24 D E