

6	(a)	(i)	Increasing R increases the total resistance of the circuit, thus reducing the current in the circuit. Thus the potential drop across the internal resistance is reduced. Since the terminal p.d. is the e.m.f. of the battery minus the p.d. across the internal resistance, terminal p.d. increases with R. OR Increasing R increases the external resistance. This increases the ratio of the external resistance to the total resistance. By the potential divider principle, the terminal p.d. increases with R.	[1] [1] [1] [1] [1] [1]
	(a)	(ii)	$I = \frac{25.2}{2.00 + 4.00 + 40.0} = 0.548 \text{ A}$ $V_B = 25.2 - 0.548(2.00)$ $= 24.1 \text{ V}$ OR $V_B = \frac{4.00 + 40.0}{2.00 + 4.00 + 40.0} \times 25.2$ $= 24.1 \text{ V}$	[1] [1] [1] [1]
	(b)	(i)	$V_R = (1.60 \times 10^{-3})(1.50 \times 10^3) = 2.40 \text{ V}$ $V_{\text{thermistor}} = 6.00 - 2.40 = 3.60 \text{ V and } R_{\text{thermistor}} = \frac{3.60}{1.60 \times 10^{-3}} = 2250 \Omega$ From the graph, $t = 14^\circ\text{C}$	[1] [1] [1]
	(b)	(ii)	From the graph, $R_{\text{thermistor}} = 3100 \Omega$ at $t = 5^\circ\text{C}$ Based on potential divider principle, potential difference across the fixed resistor $V_R = \left(\frac{1500}{1500 + 3100} \right) 6.00 = 1.96 \text{ V}$	[1] [1]