

21 ANS: B

When the current is in the positive direction, the diode allows it to flow through the NTC thermister. The upper portion of the graph is slightly decreasing in gradient due to the properties of the thermistor.

When the current flows in the opposite direction, the diode prevents it from passing through the bulb. It flows through the other branch of the parallel connection instead. A resistor obeys Ohm's law so current varies proportionally to the voltage.