

4	(a)	(i)	$R = \frac{\rho l}{A} = \frac{1.1 \times 10^{-6} \times 98}{\pi \left(\frac{1.1 \times 10^{-3}}{2} \right)^2}$ $= 113 \, \Omega$	A1
		(ii)	As the wire stretches, its length increases and its cross sectional area decreases. From $R = \frac{\rho l}{A}$, R will increase.	B1
	(b)	(i)	$R_{PQ} = 1\% \times 113 = 1.13 \, \Omega$ $V_{PQ} = \frac{R_{PQ}}{R_{PQ} + R + r} \times E_1$ $V_{PQ} = \frac{1.13}{1.13 + R + r} \times E_1$ $V_{PQ} \text{ per unit length}$ $= \frac{\frac{1.13}{1.13 + R + r} \times E_1}{0.98}$ $= \frac{1.15}{1.13 + R + r} \times E_1$	M1 C1 for correct R and length of PQ A1
			1. Length PJ = $\frac{1}{3} \times 0.98 = 0.327 \text{ m}$ Using (b)(i) ans, $V_{PJ} = 0.327 \times \frac{1.15}{1.13 + R + r} \times E_1$ $= 0.327 \times \frac{1.15}{1.13 + 1.0 + r} \times 12$ At balanced length, $V_{PJ} = E_2$ $0.327 \times \frac{1.15}{1.13 + 1.0 + r} \times 12 = 1.5$ $r = 0.878 \, \Omega$	C1 C1 A1
			2. If the resistance R is too high, the pd across the PQ will be too low. If the p.d. across PQ is lower than the e.m.f. of E_2 , there will be no balance point.	B1 B1