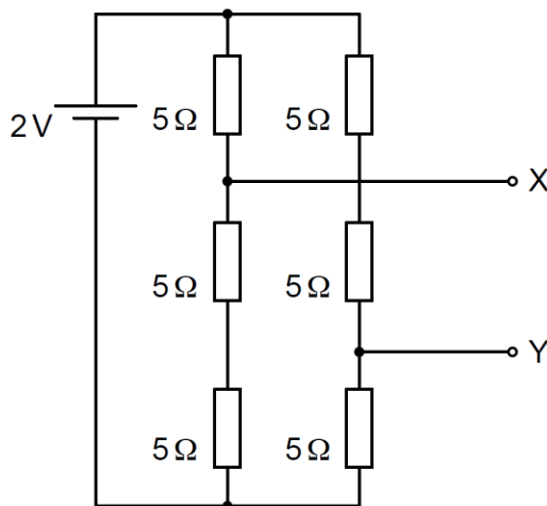


- 23** Six resistors, each of resistance $5\ \Omega$, are connected to a $2\ \text{V}$ cell of negligible internal resistance.



What is the potential difference between terminals X and Y?


A $\frac{2}{3}\ \text{V}$

B $\frac{8}{9}\ \text{V}$

C $\frac{4}{3}\ \text{V}$

D $2\ \text{V}$

Ans: A

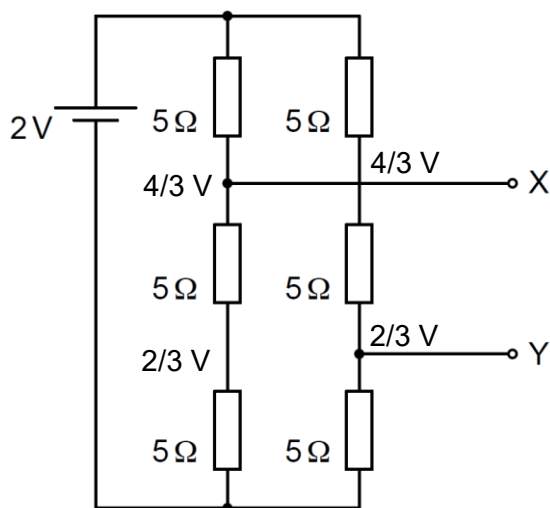

$$\Delta = \frac{4}{3} - \frac{2}{3} = \frac{2}{3}\ \text{V}$$