
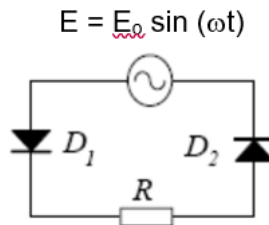


Ans: C

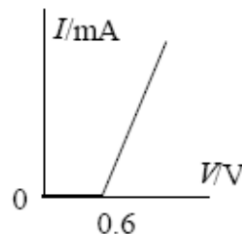- 26** The circuit below shows the rectification of a sinusoidal a.c. supply using two identical diodes D_1 and D_2 .



Each of the diodes has the I - V characteristics as shown.



For a current to flow through R , the value of E_0 must be at least

A 0.3 V

B $0.3\sqrt{2}$ V

C $0.6\sqrt{2}$ V

D $1.2\sqrt{2}$ V

	Ans: D
	For A, B and C, the value of E can never be 1.2 V. So cannot be the answer.

27	Which piece of evidence about the photoelectric effect cannot be explained using a wave
----	---