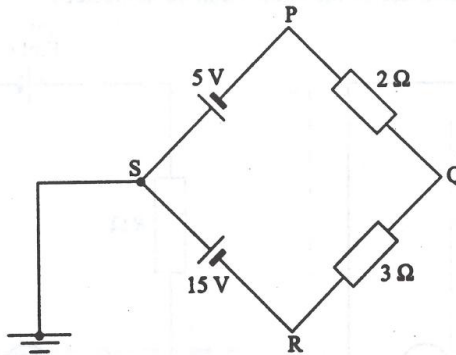


Ans: C

21 In the circuit below, the point S is earthed.

12



The electric potential at the points **P**, **Q** and **R** respectively are

	Potential at P	Potential at Q	Potential at R
A	-5V	-15V	-10V
B	10V	1V	-15V
C	-5V	-9V	-15V
D	5V	-1V	10V

Ans: C

Potential at P is lower than that of S by 5V

Potential at Q is lower than that of S by 15V

Current in circuit = $\frac{15 - 5}{2 + 3} = 2 \text{ A}$ and it runs clockwise in the circuit.

Potential at P = $-5 - (2 \times 2) = -9$

22. An alpha particle initially at rest is accelerated across a potential difference 250 V before entering