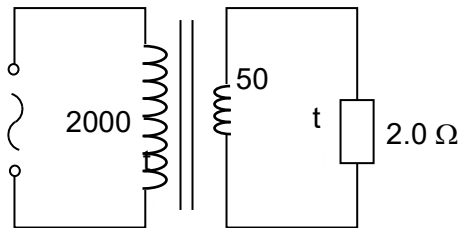


Answer : C

- 25** In the diagram shown, the **average** power dissipated across a $2.0\ \Omega$ resistor is $50\ \text{W}$.



What is the peak potential difference across the primary coil of the ideal transformer?

- A** $20\ \text{V}$ **B** $40\ \text{V}$ **C** $400\ \text{V}$ **D** $564\ \text{V}$

Answer: D

- 26** A source emits monochromatic light of frequency $5.0 \times 10^{14}\ \text{Hz}$ at a rate of $0.10\ \text{W}$. The