

21 Answer: D

Effective resistance between PQ has to be lowest

A: 5 Ω

B: 2.67 Ω

C: 1.2 Ω

D: 0.5 Ω