

- 4 (a) (i) From the graph, $R = 80 \, \Omega$, $T = 40 \, \Omega$, [1]

$$E = I R_T$$

$$3.0 = I (80 + 40)$$

$$I = 25 \times 10^{-3} \, \text{A} \quad [1]$$

- (ii) (When the temperature increases from 0°C to 75°C , the resistance of R increases slowly compared to resistance of T, which is decreasing more rapidly, thus,) the effective (or total) resistance decreases at a decreasing rate. [1]

{Students who do not describe how the rate of effective resistance changes will only get 0 m}

- (iii) From the graph at 30°C ,
resistance of $R = 55 \, \Omega$ and resistance of $T = 110 \, \Omega$
[1 m for both correct. Accept $\pm 5 \, \Omega$]

Using potential divider rule,

$$\text{p.d. across } T = 110 / (110 + 55) \times 3.0 \, \text{V} = 2.0 \, \text{V} \quad [1]$$

- (b) (i) Resistance of wire $= \rho L / A$
 $= 1.20 \times 10^{-6} \times 1.20 / [\pi \times (0.200 \times 10^{-3})^2]$ [1]
 $= 11.46 \, \Omega$ (accept 3 or 4 sf) [1]

- (ii) p.d. across XY, $V_{XY} = [11.46 / (11.46 + 1.0 + 5.0)] \times 9.0$
 $= 5.907 \, \text{V}$ [1]

At balance point, p.d. across XJ = p.d. across thermistor = $2.0 \, \text{V}$ (from aiii)

Therefore, $XJ / XY = V_{XJ} / V_{XY}$

$$XJ / 1.20 = 2.0 / 5.907$$

$$XJ = 0.406 \, \text{m} \quad [1, \text{ECF from part (aiii)}]$$

- (iii) When the temperature is at 75°C , the resistances of R and T are equal, the p.d. across thermistor will decrease (to $1.5 \, \text{V}$). Hence, the balance length XJ will be shorter. [1]