

21. B

if current in Y is I , then current in F is $2I$, so current in C is $3I$

$R_{AB} = 2/(1+2) = 2/3 R$, so $R_{C+AB+D} = 1 + 2/3 + 1 = 8/3 R$

since current in R_{C+AB+D} is $3I$, then current in E is $8I$

so current in X = $3I + 8I = 11I$

