

22 C To turn on both diodes D_1 and D_2 so that they are forward-biased, V_0 must be more than $(0.3 + 0.7) \text{ V} = 1.0 \text{ V}$.