

Q20 Ans: A

Power dissipated, $P = \frac{V^2}{R}$

Since the resistors are identical, $P \propto V^2$

R and Q are connected in parallel, hence

$$\begin{array}{ccc} V_S : V_R : V_Q & \text{or} & V_S^2 : V_R^2 : V_Q^2 \\ 2 : 1 : 1 & \text{or} & 4 : 1 : 1 \end{array}$$

Power dissipated across R = $\frac{1}{6} \times 12 = 2 \text{ W}$

Q21 Ans: D