

Q21 Ans: D

When the switch is closed, the p.d. across the parallel resistors will decrease. Hence the potential at **P** will decrease. The p.d. across the right resistor will increase, hence potential at **Q** will decrease to a more negative value.

Q22 Ans: D